


EL32. Adaptateurs d'impédance à composants réactifs

NB: Cas simple d'adaptation d'impédance:

$$P_u = \frac{u^2}{R_u} = e_g^2 \frac{R_{ue}}{(R_u + R_g)^2}$$

$$\frac{dP_u}{dR_u} = e_g^2 \frac{(R_u + R_g)^2 - 2R_{ue}(R_u + R_g)}{(R_u + R_g)^4}$$
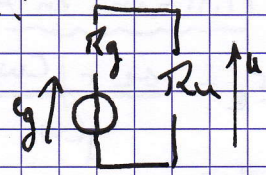
$$= e_g^2 \frac{-R_{ue}}{(R_u + R_g)^3} = 0 \text{ si } R_{ue} = R_g$$



Structure a: $Z_a = Z_c + \frac{Z_L R_u}{Z_L + R_u} = \frac{1}{j\omega C} + \frac{j\omega L R_u}{j\omega L + R_u}$

$$\rightarrow Z_a = \frac{-j}{\omega C} + \frac{j\omega L R_u (R_u - j\omega L)}{R_u^2 + (\omega L)^2} = \frac{(\omega L)^2 R_u}{R_u^2 + (\omega L)^2} + j \left(\frac{R_u^2 \omega L}{R_u^2 + (\omega L)^2} - \frac{1}{\omega C} \right)$$

Adaptation d'impédance $Z_a = R_g \Rightarrow$

$$\begin{cases} R_g = R_u \frac{(\omega L)^2}{R_u^2 + (\omega L)^2} & (a) \\ \frac{R_u^2 \omega L}{R_u^2 + (\omega L)^2} = \frac{1}{\omega C} & (b) \end{cases}$$

(a): $\Rightarrow R_u > R_g$

$R_u(a) - L\omega(b): R_u R_g = \frac{L\omega}{C} \Rightarrow \frac{R_u R_g}{L\omega} = \frac{1}{C} \quad (c)$

Dans (b): $\frac{R_u^2 \omega L}{R_u^2 + (\omega L)^2} = \frac{R_u R_g}{L\omega} \rightarrow (\omega L)^2 = \frac{R_u^2 R_g}{R_u - R_g} \rightarrow L = \frac{R_u}{\omega} \sqrt{\frac{R_g}{R_u - R_g}}$

Avec (c): $C = \frac{L}{R_u R_g} \Rightarrow C = \frac{1}{R_g \omega} \sqrt{\frac{R_g}{R_u - R_g}}$

Structure b: $Z_b = Z_c \parallel (Z_L + R_u) = \frac{j\omega L (R_u + \frac{1}{j\omega C})}{j\omega L + R_u + \frac{1}{j\omega C}} = \frac{\frac{L}{C} + jL R_u \omega}{R_u + j(\omega L - \frac{1}{\omega C})}$

$$Z_b = \frac{(\frac{L}{C} + jL R_u \omega)(R_u - j(\omega L - \frac{1}{\omega C}))}{R_u^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{\frac{L R_u}{C} + L R_u \omega ()}{R_u^2 + (\omega L - \frac{1}{\omega C})^2} + j \frac{L R_u^2 \omega - \frac{L}{C} ()}{R_u^2 + ()^2} = R_g : \text{adaptation d'impédance}$$

$$\Rightarrow \begin{cases} \frac{\frac{L R_u}{C} + L R_u \omega ()}{R_u^2 + ()^2} = R_g & (a) \\ L R_u^2 \omega - \frac{L}{C} () = 0 & (b) \end{cases} \Rightarrow \begin{cases} \frac{L}{C} R_u + L R_u \omega () = R_g (R_u^2 + ()^2) & (a) \\ \frac{L}{C} () = L R_u^2 \omega & (b) \end{cases}$$

(a). () - (b) $R_u: L R_u \omega ()^2 = R_g (R_u^2 + ()^2) () - L R_u^3 \omega$

$L R_u \omega (R_u^2 + ()^2) = R_g () (R_u^2 + ()^2)$

$L \omega R_u = R_g (L \omega - \frac{1}{C \omega}) \Rightarrow L \omega (R_u - R_g) = -\frac{R_g}{C \omega}$

$$\rightarrow \underline{R_u < R_g} ; \quad \underline{L\omega = \frac{R_g}{R_g - R_u} \frac{1}{C\omega}}$$

$$L\omega - \frac{1}{C\omega} = \left(\frac{R_g}{R_g - R_u} - 1 \right) \frac{1}{C\omega} \rightarrow L\omega - \frac{1}{C\omega} = \frac{1}{C\omega} \frac{R_u}{R_g - R_u}$$

$$\text{Dams (b): } \frac{L}{C^2\omega} \frac{R_u}{R_g - R_u} = L R_u \omega \Rightarrow \underline{C = \frac{1}{\omega} \sqrt{\frac{1}{R_u(R_g - R_u)}}}$$