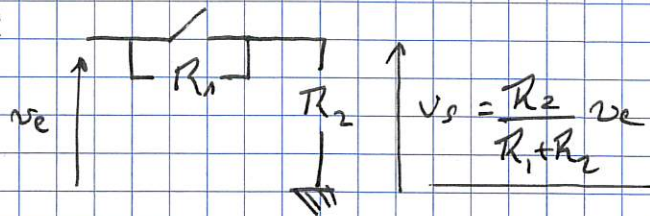
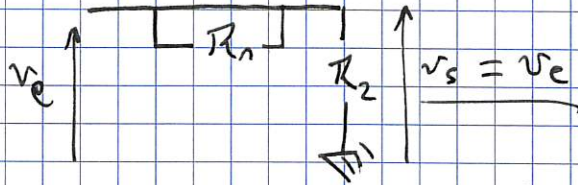


EL 44 - Filtre du 1^{er} ordre

La BF: schéma équivalent :


$$H\bar{F}:$$


b.  Pont diviseur de tension: $\frac{v_s}{v_e} = \frac{R_2}{R_2 + Z_n}$
 où $Z_n = \frac{R_n / j\omega C_n}{R_n + \frac{1}{j\omega C_n}}$

$$= \frac{R_n}{1 + jR_n C_n \omega}$$

$$\Rightarrow \underline{H} = \frac{R_2}{R_2 + \frac{R_1}{1+j\omega R_1 C_1}} = R_2 \frac{1+j\omega R_1 C_1}{R_2(1+j\omega R_1 C_1) + R_1}$$

$$= \frac{R_2}{R_1 + R_2} \frac{1+j\omega R_1 C_1}{1 + j\omega R_1 C_1 \frac{R_2}{R_1 + R_2}} \Rightarrow$$

où $u = R_1 C_{uv}$

$$\alpha = \frac{R_2}{R_1 + R_2} = 1,0 \cdot 10^{-2}$$

$$\tau = \alpha R_1 C = 4,7 \cdot 10^{-6} \text{ s}$$

$$H = \alpha \frac{1 + j \frac{\omega}{\omega_0}}{1 + j \frac{\omega}{\omega_1}}$$


c. BF: $\omega \tau \ll 1$: $\frac{H}{12} \propto \tau$

H.F.: $\omega \tau \gg 1$: $\underline{H} \approx 1$ $\therefore$


$$\varphi = \arg(H) = \arctan\left(\frac{Iw}{R}\right) - \arctan(Iw)$$

BF. $\varphi \sim 0$

$$HF: \psi \approx 0$$

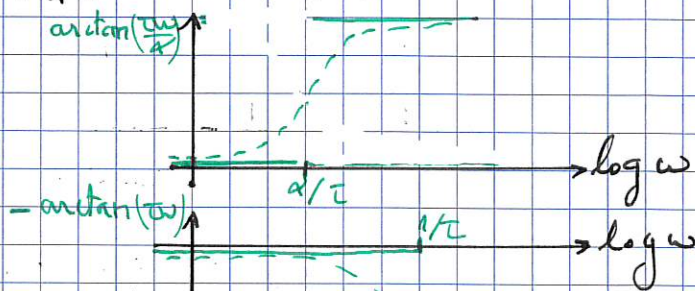

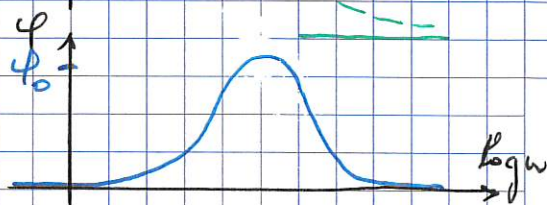Donc graphiquement, ϕ passe
par un maximum.



$$\frac{d\varphi}{d\omega} = \frac{\frac{\tau}{\alpha}}{1 + \left(\frac{\tau\omega}{\alpha}\right)^2} - \frac{\tau}{1 + (\tau\omega)^2} = \frac{\frac{\tau}{\alpha}(1 + (\tau\omega)^2) - \tau(1 + \left(\frac{\tau\omega}{\alpha}\right)^2)}{(1 + \left(\frac{\tau\omega}{\alpha}\right)^2)(1 + (\tau\omega)^2)}$$


Numerateur : $\frac{\tau}{\alpha} - \tau + \left(\frac{\tau}{\alpha} - \frac{\tau}{\alpha^2}\right)(\tau\omega)^2 = \left(\frac{\tau}{\alpha} - \tau\right)\left(1 - \frac{1}{\alpha}(\tau\omega)^2\right)$
 s'annule pour $\omega = \frac{\sqrt{\alpha}}{\tau}$ $\omega = 2,1 \cdot 10^4 \text{ rad s}^{-1}$

$$\varphi_0 = \varphi\left(\frac{\sqrt{\alpha}}{\tau}\right) = \arctan\left(\frac{1}{\sqrt{\alpha}}\right) - \arctan(\sqrt{\alpha}) \quad \varphi_0 = 1,37 \text{ rad}$$

b - $\omega \leq \frac{\alpha}{\tau} \ll \frac{1}{\tau}$: $H \approx \alpha \Rightarrow G_{dB} \approx 20 \log \alpha$

* $\frac{\alpha}{\tau} \ll \omega \leq \frac{1}{\tau}$: $H \approx \tau\omega \Rightarrow G_{dB} \approx 20 \log \tau + 20 \log \omega$

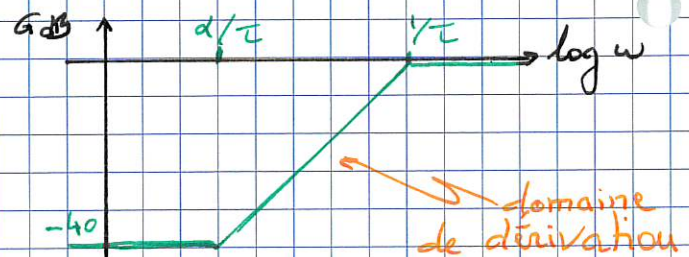* $\omega \gg \frac{1}{\tau} \gg \frac{\alpha}{\tau}$: $H \approx 1 \Rightarrow G_{dB} \approx 0$



$$\omega_1 = \frac{\alpha}{\tau} = 2,1 \cdot 10^3 \text{ rad s}^{-1} \rightarrow f_1 = 3,4 \cdot 10^2 \text{ Hz}$$

$$\omega_2 = \frac{1}{\tau} = 2,1 \cdot 10^5 \text{ rad s}^{-1} \rightarrow f_2 = 34 \text{ kHz}$$

3 a - Couplage DC pour visualiser l'offset.

b - $\omega \leq \omega_1$: signal très atténué non déformé

c - $\omega_1 \leq \omega \leq \omega_2$: signal intégré et atténué

